

Expt. No: 3
Date: 14.2.2023

Hariharan A
203002034

Design and Synthesis of Carry Lookahead Adders

Aim:

- To model a 4-bit Carry Lookahead Adder using Dataflow modeling.
- To compile, simulate and plot the results using Xilinx ISE Tools.
- To implement the proposed systems using Xilinx Tools and generate the synthesis report.

Software used:

Xilinx ISE Tools

Functional Description:

Full Adder:

Truth Table

A	B	Carry-in	Sum	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Equation:

Inputs: A, B & Cin

Outputs: Carry generate: $G_i = A(i) \& B(i)$

Carry propagate: $P_i = A(i) \wedge B(i)$


Sum: $S_i = P(i) \wedge C(i)$

Carry output: $C(i+1) = G(i) + P(i) \& C(i)$


where i-bit position

Full adder:


Block Diagram:

 

Logic Diagram:

 


4-Bit Carry Lookahead Adder:

 

Schematic Diagram:

4-Bit Carry Lookahead Adder:

 

Modeling using Verilog HDL:

4-Bit Carry Lookahead Adder:

Design module:

```
module CLA_Adder(a,b,cin,sum,cout);  
input[3:0] a,b;  
input cin;  
output[3:0] sum;  
output cout;  
wire[3:0] p,g,c;  
assign p[3:0]=a[3:0]^b[3:0];  
assign g[3:0]=a[3:0]&b[3:0];  
assign c[0]=cin;  
assign c[3:1]=g[2:0]|(p[2:0]&c[2:0]);  
assign cout=c[3];  
assign sum[3:0]=p[3:0]^c[3:0];  
endmodule
```

endmodule

Stimulus file:

```


module test_cla;
    // Inputs
    reg [3:0] A;
    reg [3:0] B;
    reg CIN;
    // Outputs
    wire [3:0] SUM;
    wire COUT;
    // Instantiate the Unit Under Test (UUT)
    CLA_Adder uut(A,B,CIN,SUM,COUT);
    //Print statement
    initial begin
        $monitor($time," A= %b,B=%b,CIN= %b,COUT= %b, SUM= %b",A,
B, CIN, COUT, SUM);
    end
initial begin
    A = 4'd0; B = 4'd0; CIN = 1'b0;
    #100 A= 4'd3; B= 4'd4;
    #100 A= 4'd3; B= 4'd4;
    #100 A = 4'd5; B = 4'd5;
    #100 A = 4'd9; B = 4'd9;
    #100 A = 4'd3; B= 4'd12;
    #100 A = 4'd10; B = 4'd14; CIN = 1'b1;
end
endmodule

```

Simulation Results:

Name	Value	
SUM[3:0]	1001	0000 0111 1001 1010 0010 1111 1001
COUT	1	
A[3:0]	1010	0000 0011 0101 1001 0011 1010
B[3:0]	1110	0000 0100 0101 1001 1100 1110
CIN	1	

RTL Schematic Diagram:

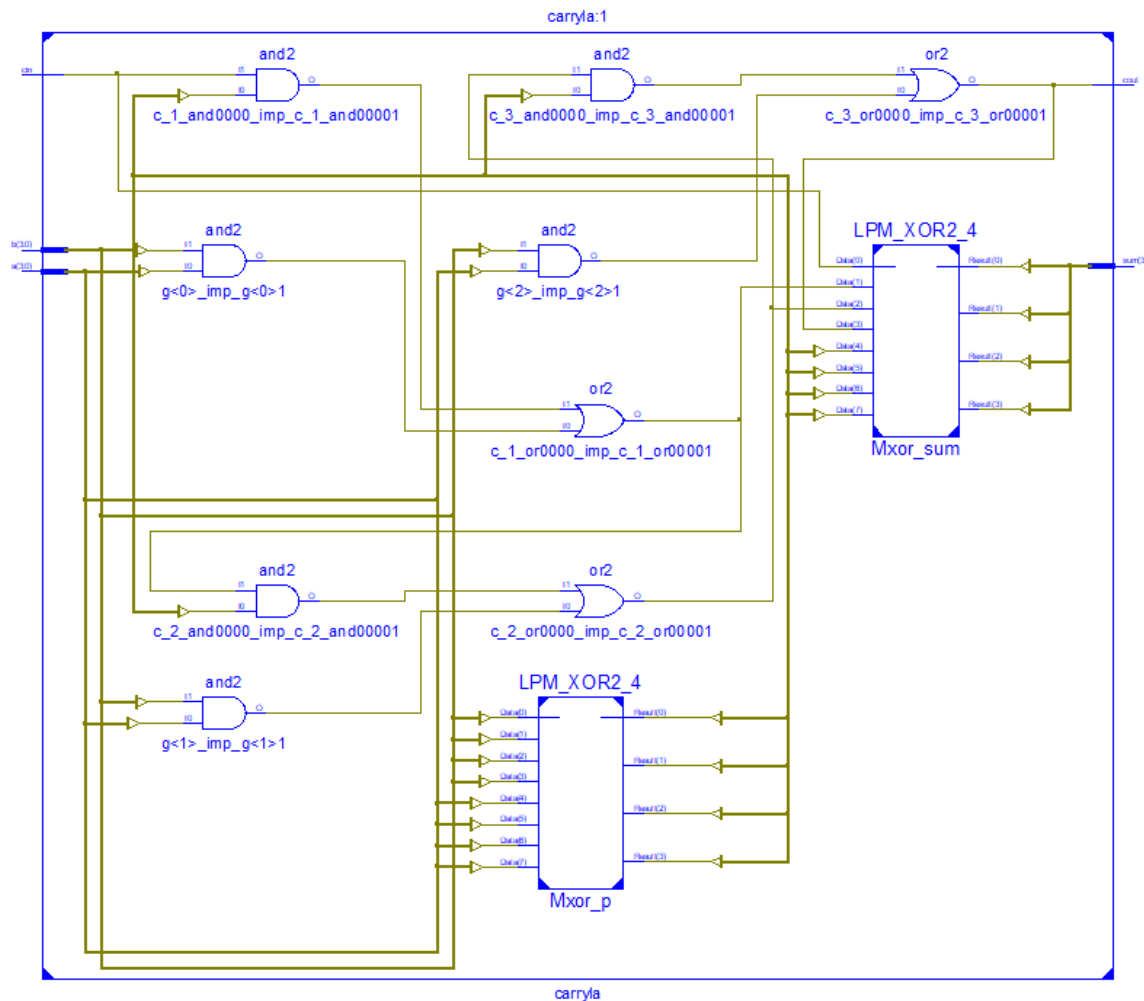

Design Summary:

Device Utilization Summary			
Logic Utilization	Used	Available	Utilization
Number of 4 input LUTs	7	4,896	1%
Number of occupied Slices	5	2,448	1%
Number of Slices containing only related logic	5	5	100%
Number of Slices containing unrelated logic	0	5	0%
Total Number of 4 input LUTs	7	4,896	1%
Number of bonded IOBs	14	158	8%
Average Fanout of Non-Clock Nets	1.63		

Result:

Thus, a model for 4-bit Carry Lookahead Adder using Dataflow modelling was compiled, simulated, synthesized, and implemented.