

Ex No: 05

Date:

4-BIT UP/DOWN SYNCHRONOUS COUNTER USING D-FLIP FLOP

AIM:

To design and implement a 4-bit Up/Down Synchronous Counter using Cadence Virtuoso 180nm CMOS technology.

TOOLS REQUIRED:

Cadence Virtuoso Analog Design Environment

PROCEDURE:

- Open Virtuoso and create a new library with existing gpd090nm technology.
- File -> New -> Cellview -> Schematic
- With the help of the circuit diagram, implement the D-Flip Flop using cmos by adding instances and connect the instances using wire
- Add the source and ground to the required pins
- Complete the circuit with the wireconnections
- Launch ->ADE L
- Choose Transient analysis
 - Set the stop time
 - Click on moderate
- Select input and output pins from the design by clicking on the corresponding wires
- Then run the simulation process to get the transient response
- Thus, the pre layout simulation results are obtained.

CIRCUIT DIAGRAM:

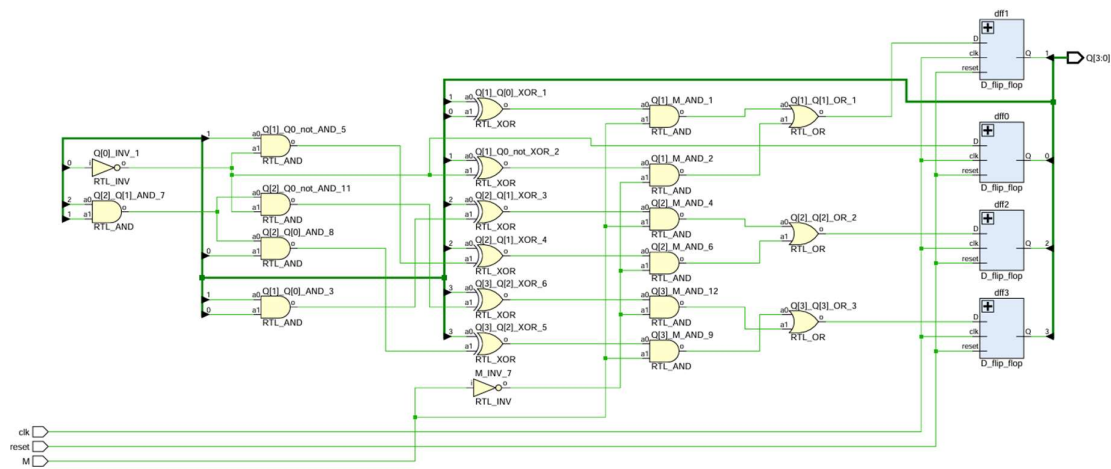


Fig 5.1 Circuit diagram of 4 bit synchronous up/down counter

STATE DIAGRAM:

 


Fig 5.2 State diagram of 4 bit synchronous up/down counter

TRANSIENT ANALYSIS:

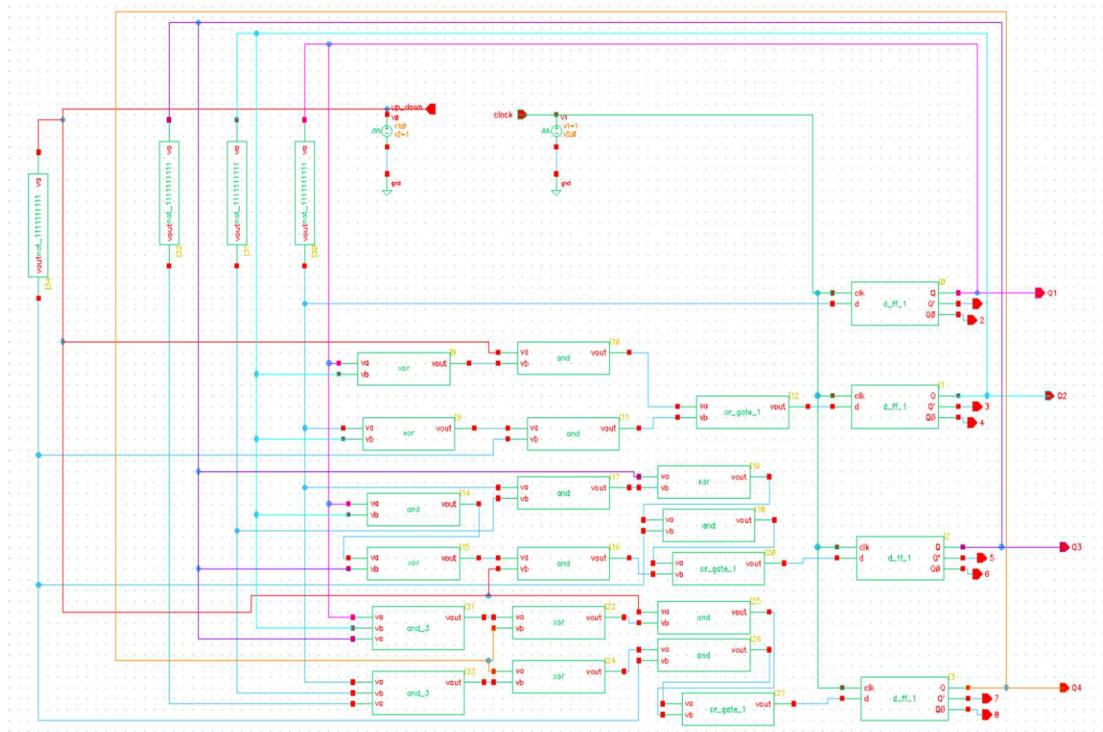


Fig 5.3 Schematic Diagram of 4 bit synchronous up/down counter

 


Fig 5.4 Transient Analysis of 4 bit synchronous up/down counter

RESULT:

Thus, the 4 bit synchronous up/down counter using D flipflop was implemented and verified using Cadence Virtuoso Analog Design Environment.