

Expt. No: 2  
Date: 07.02.2023

Hariharan A  
203002034

## Design and Synthesis of Ripple Carry Adders

### Aim:

- To model a 4-bit Ripple Carry Adder and an 8-bit Ripple Carry Adder using structural modeling.
- To compile, simulate and plot the results using Xilinx ISE Tools.
- To implement the proposed systems using Xilinx Tools and generate the synthesis report.

### Software used:

Xilinx ISE Tools

### Functional Description:

#### Full Adder:

Truth Table


| A | B | Carry-in | Sum | Carry-out |
|---|---|----------|-----|-----------|
| 0 | 0 | 0        | 0   | 0         |
| 0 | 0 | 1        | 1   | 0         |
| 0 | 1 | 0        | 1   | 0         |
| 0 | 1 | 1        | 0   | 1         |
| 1 | 0 | 0        | 1   | 0         |
| 1 | 0 | 1        | 0   | 1         |
| 1 | 1 | 0        | 0   | 1         |
| 1 | 1 | 1        | 1   | 1         |

Boolean Equation:

Inputs: A, B & Cin


Outputs: Sum:  $A \oplus B \oplus C_{in}$

 Carry:  $(A \& B) \vee (B \& C_{in}) \vee (C_{in} \& A)$



**Full Adder:**

**Logic Diagram:**

 

**4-Bit Ripple Carry Adder:**




### 8-Bit Ripple Carry Adder:




### Schematic Diagram:

#### 4-Bit Ripple Carry Adder:

 

#### 8-Bit Ripple Carry Adder:

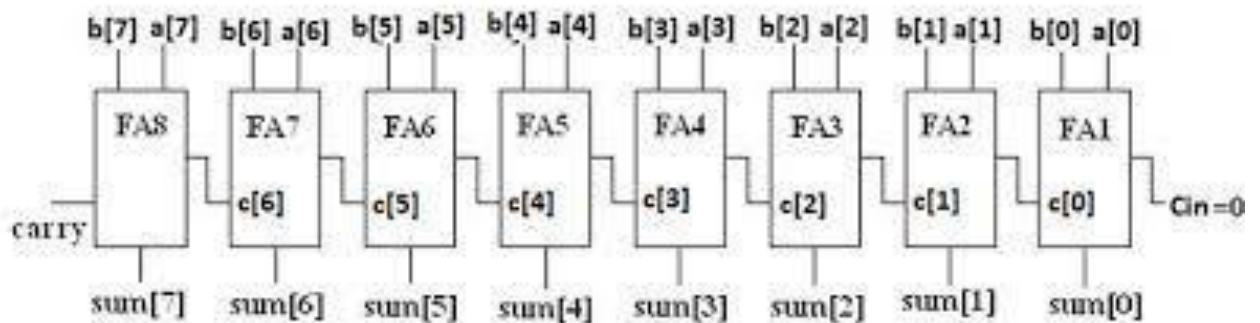

**Modelling using Verilog HDL:**

**4-Bit Ripple Carry Adder:**

**Design module:**

```
module RCA(sum,cout,a,b,cin); output [3:0] sum;
output cout; input [3:0] a,b; input cin;
wire c1,c2,c3;
fulladd f1(sum[0],c1,a[0],b[0],cin);
fulladd f2(sum[1],c2,a[1],b[1],c1);
fulladd f3(sum[2],c3,a[2],b[2],c2);

fulladd f4(sum[3],cout,a[3],b[3],c3);
endmodule
```

```
module fulladd(sum,cout,a,b,c); output sum,cout;
input a,b,c;
assign sum=a^b^c;
assign cout=(a&b)|(b&c)|(c&a);
endmodule
```

**Stimulus file:**

```
module stimulus; reg [3:0] A, B;
reg CIN;
wire [3:0] SUM; wire COUT;
RCA RippleCarryAdder(SUM, COUT,A,B,CIN);
Initial
Begin
$monitor($time," A= %b, B=%b, CIN= %b, COUT= %b, SUM= %b", A, B, CIN,
COUT, SUM);
end
```

```
Initial
Begin
A = 4'd0; B = 4'd0; CIN = 1'b0;
#10 A = 4'd3; B = 4'd4;
#10 A = 4'd2; B = 4'd5;
#10 A = 4'd9; B = 4'd9;
```

```
#10 A = 4'd10; B= 4'd5;  
#10 A = 4'd10; B = 4'd5; CIN = 1'b1;  
end  
endmodule
```

### **8-Bit Ripple Carry Adder:**

#### **Design module:**

```
module RippleCarryAdder(sum,cout,a,b,cin);  
output [7:0] sum;  
Output cout;  
Input[7:0] a,b;  
wire c1,c2,c3,c4,c5,c6,c7;  
fulladd f1(sum[0],c1,a[0],b[0],cin);  
fulladd f2(sum[1],c2,a[1],b[1],c1);  
fulladd f3(sum[2],c3,a[2],b[2],c2);  
fulladd f4(sum[3],c4,a[3],b[3],c3);  
fulladd f5(sum[4],c5,a[4],b[4],c4);  
fulladd f6(sum[5],c6,a[5],b[5],c5);  
fulladd f7(sum[6],c7,a[6],b[6],c6);  
fulladd f8(sum[7],cout,a[7],b[7],c7);  
endmodule
```

```
module fulladd (sum,cout,a,b,c);  
output sum,cout;  
input a,b,c;  
assign sum=a^b^c;  
assign cout=(a&b)|(b&c)|(c&a);  
endmodule
```

#### **Stimulus File:**

```
module stimulus;  
reg [7:0] A, B;  
reg C_IN;
```

```

wire [7:0] SUM; wire C_OUT;
RippleCarryAdder FA1_4(SUM, C_OUT, A, B, C_IN);
initial
begin
$monitor($time," A= %b,B=%b,C_IN= %b,C_OUT= %b, SUM= %b",A, B, C_IN,
C_OUT, SUM);
end

```


```

Initial
begin
A = 8'd0; B = 8'd0; C_IN = 1'b0;
#10 A = 8'd3; B = 8'd4;
#10 A = 8'd2; B = 8'd5;
#10 A = 8'd9; B = 8'd9;
#10 A = 8'd10; B= 8'd5;
#10 A = 8'd10; B = 8'd5; C_IN = 1'b1;
end
endmodule


```

## Simulation Results:

### 4-Bit Ripple Carry Adder:

 


### 8-Bit Ripple Carry Adder:

 


**RTL Schematic Diagram:**

**4-Bit Ripple Carry Adder:**

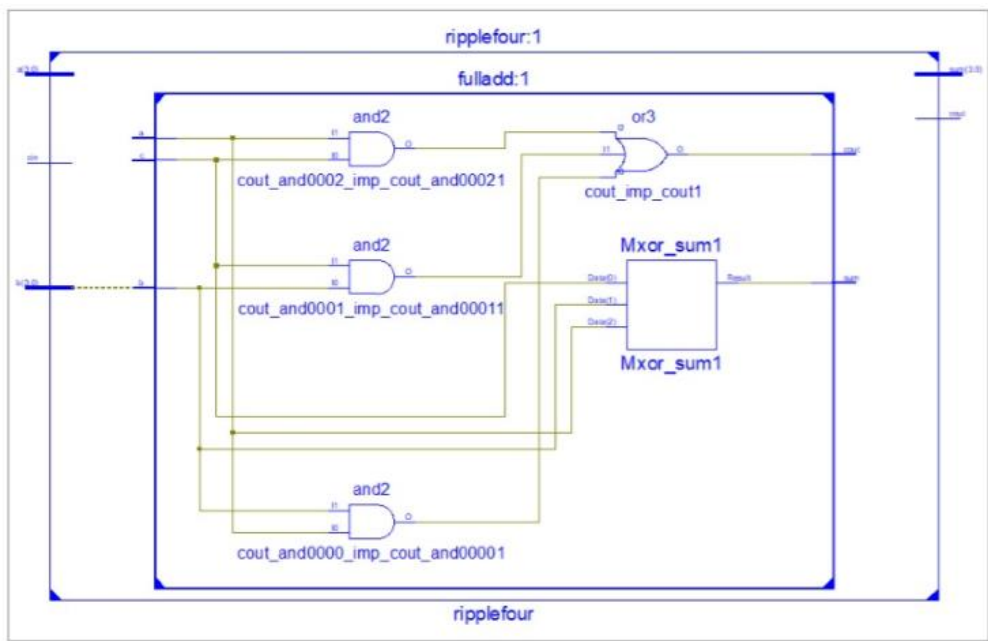

**8-Bit Ripple Carry Adder:**

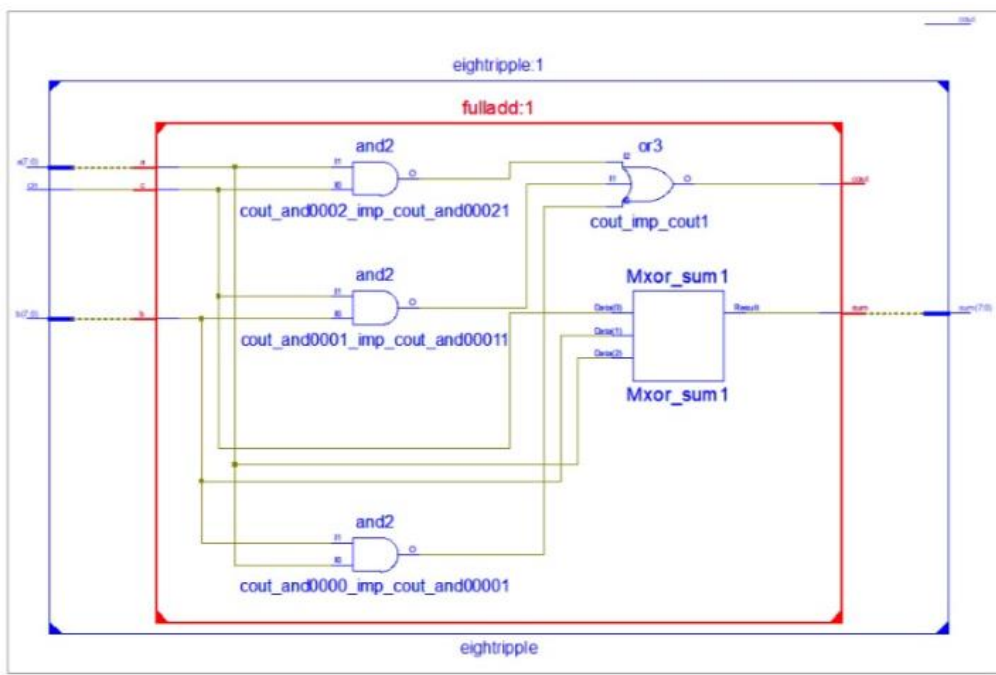

**Design Summary:**  
**4-Bit Ripple Carry Adder:**

| Device Utilization Summary                     |      |           |             |
|--|------|-----------|-------------|
| Logic Utilization                              | Used | Available | Utilization |
| Number of 4 input LUTs                         | 8    | 4,896     | 1%          |
| Number of occupied Slices                      | 6    | 2,448     | 1%          |
| Number of Slices containing only related logic | 6    | 6         | 100%        |
| Number of Slices containing unrelated logic    | 0    | 6         | 0%          |
| Total Number of 4 input LUTs                   | 8    | 4,896     | 1%          |
| Number of bonded IOBs                          | 14   | 158       | 8%          |
| Average Fanout of Non-Clock Nets               | 1.71 |           |             |

**8-bit Ripple Carry Adder:**

| Device Utilization Summary                     |      |           |             |
|--|------|-----------|-------------|
| Logic Utilization                              | Used | Available | Utilization |
| Number of 4 input LUTs                         | 16   | 4,896     | 1%          |
| Number of occupied Slices                      | 12   | 2,448     | 1%          |
| Number of Slices containing only related logic | 12   | 12        | 100%        |
| Number of Slices containing unrelated logic    | 0    | 12        | 0%          |
| Total Number of 4 input LUTs                   | 16   | 4,896     | 1%          |
| Number of bonded IOBs                          | 26   | 158       | 16%         |
| Average Fanout of Non-Clock Nets               | 1.73 |           |             |

**Result:**

Thus, a model for Ripple Carry Adder using Structural modelling was compiled, simulated, synthesized, and implemented.